

ID: _____







NAME: _____

SECTION: _____

Instruction: No marks will be awarded for Direct Answers

1. Process the **JK Latch** given below for all possible cases and fill the table accordingly?

CIRCUIT:

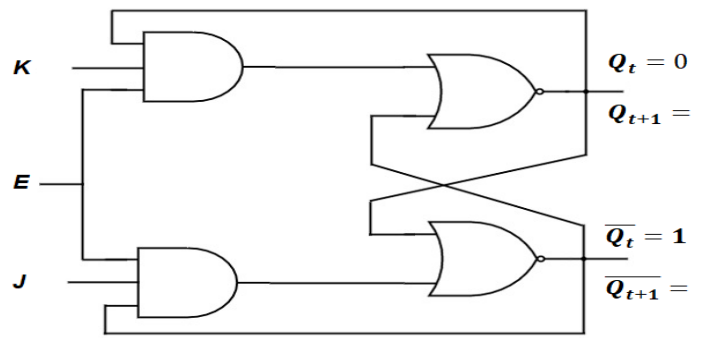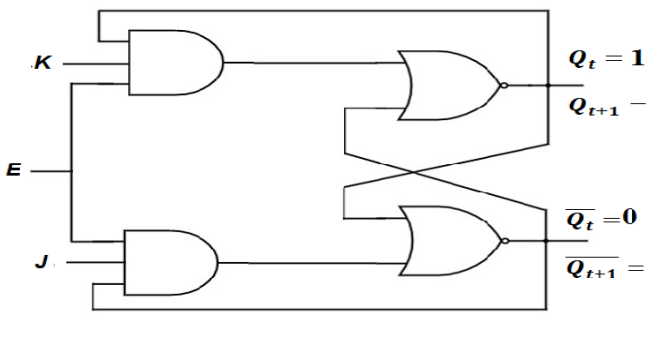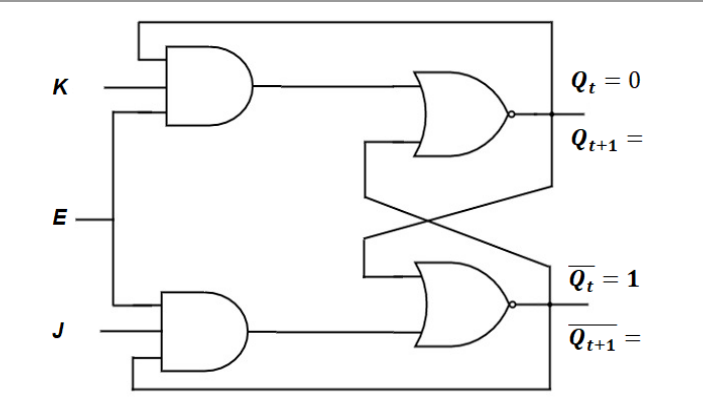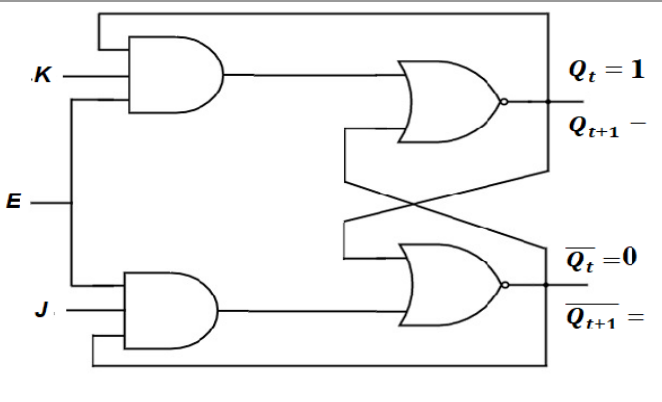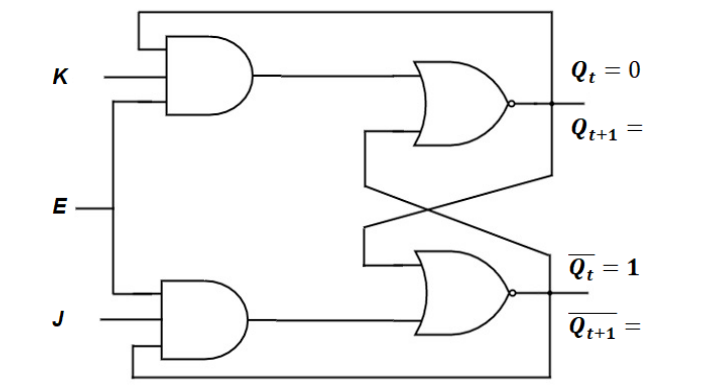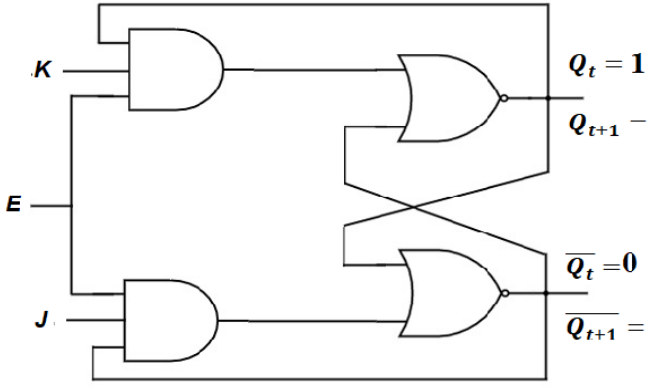Case-I ($Q_t = 0$)	Case-II ($Q_t = 1$)
$E=0, J= \quad , K= \quad , Q_t = 0, Q_{t+1} = \underline{\quad}$  $Q_t = 0$ $Q_{t+1} =$ $\overline{Q_t} = 1$ $\overline{Q_{t+1}} =$	$E=0, J= \quad , K= \quad , Q_t = 1, Q_{t+1} = \underline{\quad}$  $Q_t = 1$ $Q_{t+1} =$ $\overline{Q_t} = 0$ $\overline{Q_{t+1}} =$
$E=1, J=0, K=0, Q_t = 0, Q_{t+1} = \underline{\quad}$  $Q_t = 0$ $Q_{t+1} =$ $\overline{Q_t} = 1$ $\overline{Q_{t+1}} =$	$E=1, J=0, K=0, Q_t = 1, Q_{t+1} = \underline{\quad}$  $Q_t = 1$ $Q_{t+1} =$ $\overline{Q_t} = 0$ $\overline{Q_{t+1}} =$
$E=1, J=0, K=1, Q_t = 0, Q_{t+1} = \underline{\quad}$  $Q_t = 0$ $Q_{t+1} =$ $\overline{Q_t} = 1$ $\overline{Q_{t+1}} =$	$E=1, J=0, K=1, Q_t = 1, Q_{t+1} = \underline{\quad}$  $Q_t = 1$ $Q_{t+1} =$ $\overline{Q_t} = 0$ $\overline{Q_{t+1}} =$

QUIZ 7-A

ID: _____ NAME: _____ SECTION: _____

E=1, J=1, K=0, $Q_t = 0$, $Q_{t+1} =$ _____	E=1, J=1, K=0, $Q_t = 1$, $Q_{t+1} =$ _____
E=1, J=1, K=1, $Q_t = 0$, $Q_{t+1} =$ _____	E=1, J=1, K=1, $Q_t = 1$, $Q_{t+1} =$ _____

JK Latch						JK LATCH with SET/RESET			
E	J	K	Q_{t+1}	$\overline{Q}_{t+1}$		SET	CLEAR	Q_{t+1}	$\overline{Q}_{t+1}$
0	X	X				0	0		
1	0	0				0	1		
1	0	1				1	0		
1	1	0				1	1		
1	1	1							

2. Modify given NOR Based JK Flip Flop circuit to introduce Asynchronous **CLEAR** and **SET** inputs fill table above?

