

QUIZ 8-B (EE-1005)

ID: _____

NAME: _____

SECTION: _____

1. Draw Truth table for **T-FF** and generate Excitation table for **T-FF** and perform all required steps? [2]

2. Perform Analysis of circuit **B** given [10]