

QUIZ 9-A (Spring-2024)

ID: _____

NAME: _____

SECTION: _____

1. Design the sequential circuit using **JK-Flip-flop** following given circular sequence **2->3->5->7** back to 2? find self-correcting state **0,1** and force correction for state **4,6** to state **2** for unused state? You are required to produce state table and state equations.
Self-Correction state 0 is _____ and **state 1** _____

QUIZ 9-A (Spring-2024)

ID: _____ NAME: _____ SECTION: _____

2. For the following table, tabulate **reduce state table**. Start from state *a*, and input sequence **01110011**, determine output sequence.

Present State	Next State		Output	
	<i>x</i> = 0	<i>x</i> = 1	<i>x</i> = 0	<i>x</i> = 1
<i>a</i>	<i>f</i>	<i>b</i>	0	0
<i>b</i>	<i>d</i>	<i>c</i>	0	0
<i>c</i>	<i>f</i>	<i>e</i>	0	0
<i>d</i>	<i>g</i>	<i>a</i>	1	0
<i>e</i>	<i>d</i>	<i>c</i>	0	0
<i>f</i>	<i>f</i>	<i>b</i>	1	1
<i>g</i>	<i>g</i>	<i>h</i>	0	1
<i>h</i>	<i>g</i>	<i>a</i>	1	0

3. Design **4-bit-Universal Shift Register**? Perform following operations.

<i>S</i> ₂	<i>S</i> ₁	<i>S</i> ₀	Register Operation	<i>S</i> ₂	<i>S</i> ₁	<i>S</i> ₀	Register Operation
0	0	0	Clear to 0	1	0	0	Compliment Of Old State
0	0	1	Parallel load	1	0	1	Shift Left
0	1	0	Shift Right	1	1	0	Compliment of Parallel load
0	1	1	No Change	1	1	1	Clear to 1