
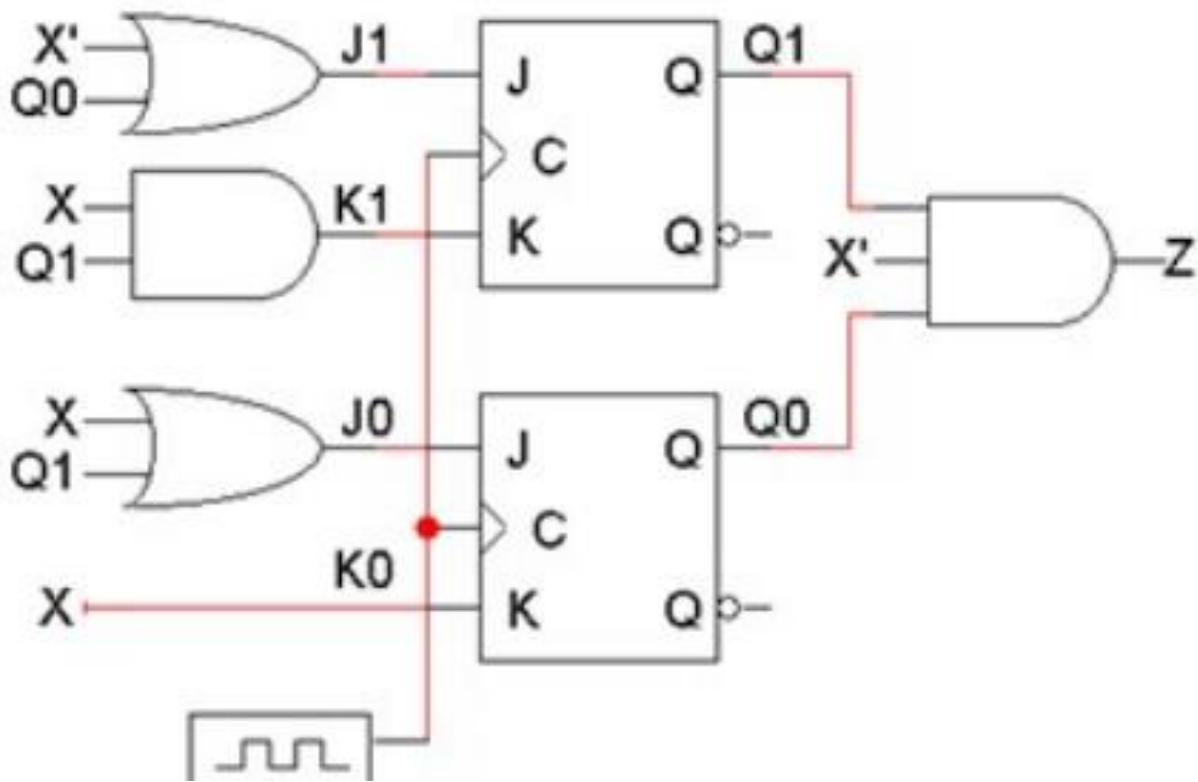


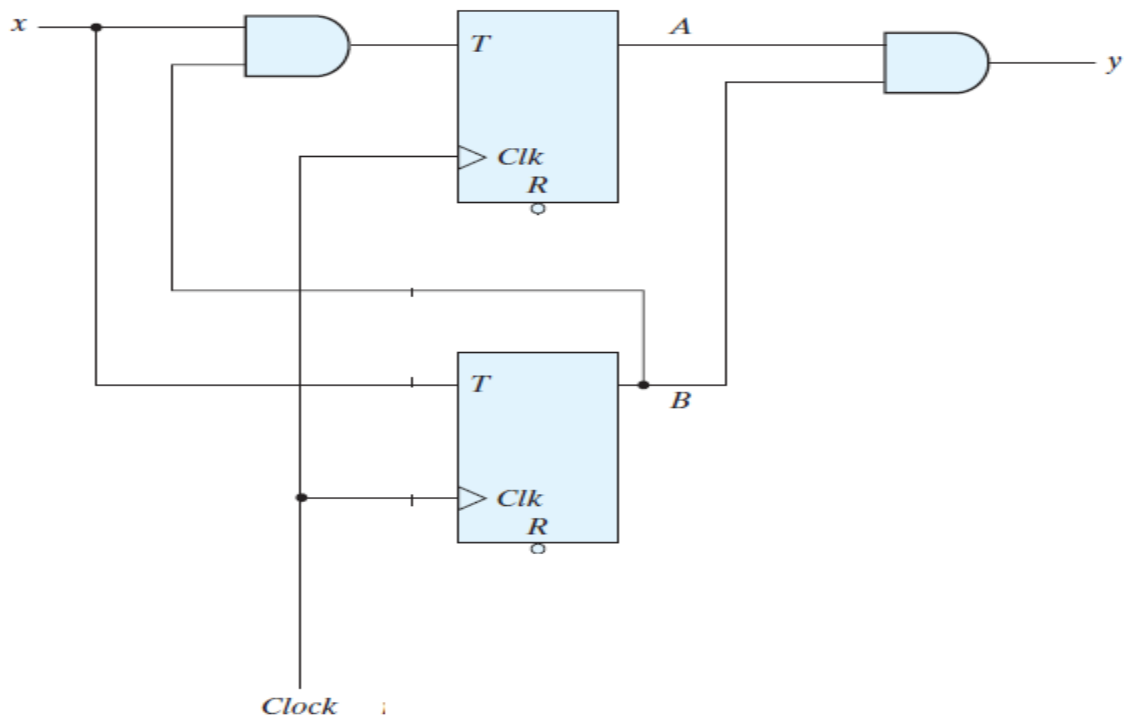
Analyse the following circuit A and Generate state table and State diagram



Analyse the following circuit B and Generate state table and State diagram



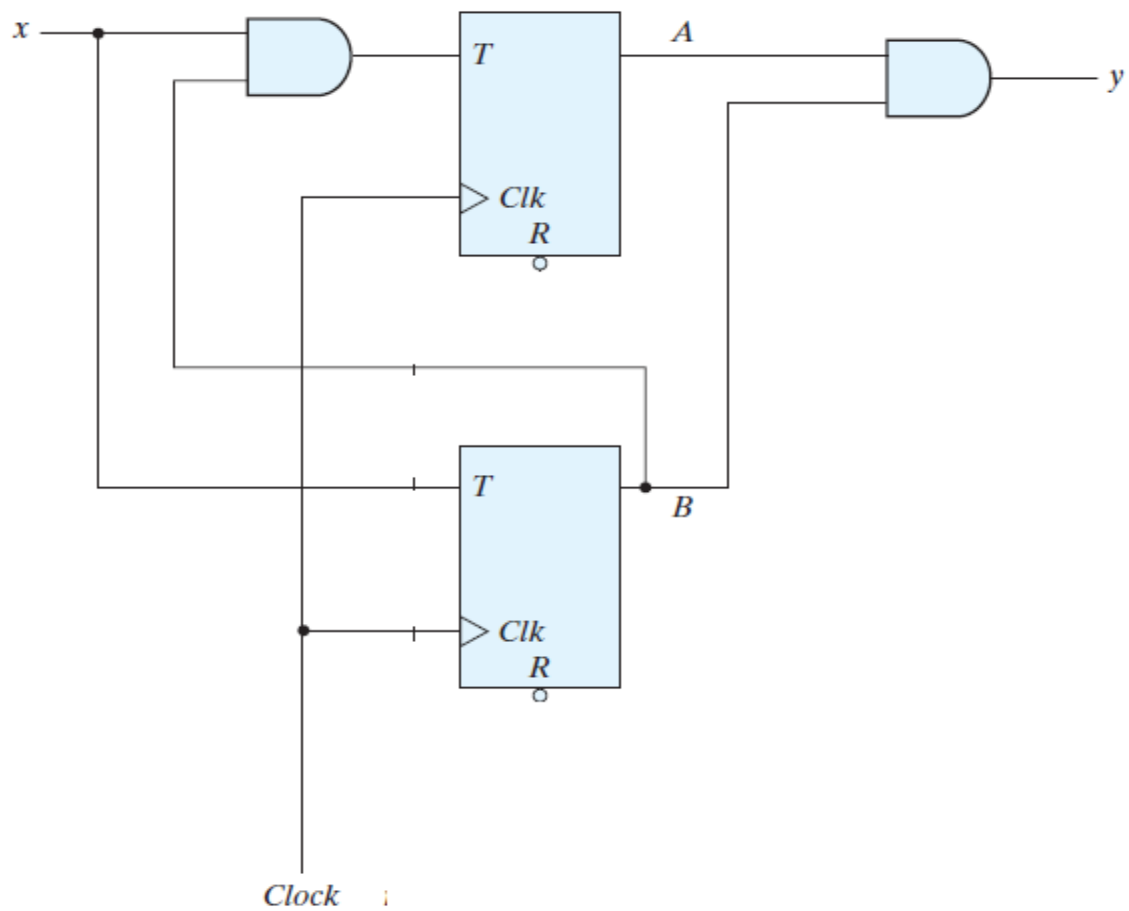Analyse the following circuit B and Generate state table and State diagram



Analyse the following circuit A and Generate state table and State diagram

