





Digital Design & Computer Architecture

Sarah Harris & David Harris

Chapter 5: Digital Building Blocks

Chapter 5 :: Topics

- Introduction
- Arithmetic Circuits
- Number Systems
- Sequential Building Blocks
- Memory Arrays
- Logic Arrays

    Application Software	
Operating Systems	
Architecture	
Micro-architecture	
Logic	
Digital Circuits	
Analog Circuits	
Devices	
Physics	

Introduction


- **Digital building blocks:**
 - Gates, multiplexers, decoders, registers, arithmetic circuits, counters, memory arrays, logic arrays
- **Building blocks demonstrate hierarchy, modularity, and regularity:**
 - Hierarchy of simpler components
 - Well-defined interfaces and functions
 - Regular structure easily extends to different sizes
- **We'll use these building blocks in Chapter 7 to build a microprocessor**

Chapter 5: Digital Building Blocks

Adders

1-Bit Adders

Half Adder

 


A	B	C _{out}	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$S = A \oplus B$$

$$C_{out} = AB$$

Full Adder

 

C _{in}	A	B	C _{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


$$S = A \oplus B \oplus C_{in}$$

$$C_{out} = AB + AC_{in} + BC_{in}$$

Multibit Adders: CPAs

- Types of carry propagate adders (CPAs):
 - **Ripple-carry** (slow)
 - **Carry-lookahead** (fast)
 - **Prefix** (faster)
- Carry-lookahead and prefix adders faster for large adders but require more hardware

Symbol

 


Chapter 5: Digital Building Blocks

Ripple Carry Addition

Ripple-Carry Adder

 
- Chain 1-bit adders together
- Carry ripples through entire chain
- Disadvantage: **slow**



Ripple-Carry Adder Delay

$$t_{\text{ripple}} = N t_{FA}$$

where t_{FA} is the delay of a 1-bit full adder

 

Chapter 5: Digital Building Blocks

Carry Lookahead Addition

Carry-Lookahead Adder

Compute C_{out} for k -bit blocks using *generate* and *propagate* signals

Some definitions:

- Column i produces a carry out by either **generating** a carry out or **propagating** a carry in to the carry out
- Calculate generate (G_i) and propagate (P_i) signals for each column:
 - **Generate:** Column i will generate a carry out if A_i **and** B_i are both 1.

$$G_i = A_i B_i$$

- **Propagate:** Column i will propagate a carry in to the carry out if A_i **or** B_i is 1.

$$P_i = A_i + B_i$$

- **Carry out:** The carry out of column i (C_i) is:

$$C_i = A_i B_i + (A_i + B_i) C_{i-1} = G_i + P_i C_{i-1}$$

Propagate and Generate Signals



Examples: Column propagate and generate signals:

Column propagate:

$$P_i = A_i + B_i$$

Column generate:

$$G_i = A_i B_i$$

  

$$C_i = G_i + P_i C_{i-1}$$

Block Propagate and Generate

Now use column Propagate and Generate signals to compute **Block Propagate** and **Block Generate** signals for k-bit blocks, i.e.:

- Compute if a **k-bit group** will **propagate** a carry in (of the block) to the carry out (of the block)
- Compute if a **k-bit group** will **generate** a carry out (of the block)

Block Propagate and Generate



- **Example: 4-bit blocks**

- **Block propagate signal: $P_{3:0}$** (single-bit signal)

- A carry-in would propagate through all 4 bits of the block:

$$P_{3:0} = P_3 P_2 P_1 P_0$$

- **Examples:**

  

Block Propagate and Generate

- **Example: 4-bit blocks**

- **Block propagate signal: $P_{3:0}$** (single-bit signal)

- A carry-in would propagate through all 4 bits of the block:

$$P_{3:0} = P_3 P_2 P_1 P_0$$

- **Block generate signal: $G_{3:0}$** (single-bit signal)

- A carry is generated:
 - in column 3, **or**
 - in column 2 and propagated through column 3, **or**
 - in column 1 and propagated through columns 2 and 3, **or**
 - in column 0 and propagated through columns 1-3

$$G_{3:0} = G_3 + G_2 P_3 + G_1 P_2 P_3 + G_0 P_1 P_2 P_3$$

$$G_{3:0} = G_3 + P_3 [G_2 + P_2 (G_1 + P_1 G_0)]$$

Block Propagate and Generate

- **Example: 4-bit blocks**

- **Block generate signal: $G_{3:0}$** (single-bit signal)

- A carry is: generated in column 3, **or** generated in column 2 and propagated through column 3, **or** ...

$$G_{3:0} = G_3 + G_2P_3 + G_1P_2P_3 + G_0P_1P_2P_3$$

Carry-out (C_3) ↓ 10011 1001 + 1100 0110 1101 1000 $G_{3:0} = 1$	$C_3, C_2, C_1, C_0, C_{-1}$ $A_{3:0}$ $B_{3:0}$ $S_{3:0}$ P_3, P_2, P_1, P_0 G_3, G_2, G_1, G_0	Carry-out (C_3) ↓ 11000 1110 + 0100 0010 1110 0100 $G_{3:0} = 1$	$C_3, C_2, C_1, C_0, C_{-1}$ $A_{3:0}$ $B_{3:0}$ $S_{3:0}$ P_3, P_2, P_1, P_0 G_3, G_2, G_1, G_0	Carry-out (C_3) ↓ 01101 0110 + 0010 1000 0110 0010 $G_{3:0} = 0$	$C_3, C_2, C_1, C_0, C_{-1}$ $A_{3:0}$ $B_{3:0}$ $S_{3:0}$ P_3, P_2, P_1, P_0 G_3, G_2, G_1, G_0
---	--	---	--	---	--

Block Propagate and Generate

- **Example: 4-bit blocks**

- **Block propagate signal: $P_{3:0}$** (single-bit signal)

- A carry-in would propagate through all 4 bits of the block:

$$P_{3:0} = P_3 P_2 P_1 P_0$$

- **Block generate signal: $G_{3:0}$** (single-bit signal)

- A carry is generated:
 - in column 3, **or**
 - in column 2 and propagated through column 3, **or**
 - in column 1 and propagated through columns 2 and 3, **or**
 - in column 0 and propagated through columns 1-3

$$G_{3:0} = G_3 + G_2 P_3 + G_1 P_2 P_3 + G_0 P_1 P_2 P_3$$

$$G_{3:0} = G_3 + P_3 [G_2 + P_2 (G_1 + P_1 G_0)]$$

$$\boxed{C_3 = G_{3:0} + P_{3:0} C_{-1}}$$

Block Propagate and Generate


- **Example:** Block propagate and generate signals for 4-bit blocks ($P_{3:0}$ and $G_{3:0}$):

$$P_{3:0} = P_3 P_2 P_1 P_0$$

$$G_{3:0} = G_3 + P_3 (G_2 + P_2 (G_1 + P_1 G_0))$$

$$C_3 = G_{3:0} + P_{3:0} C_{-1}$$

32-bit CLA with 4-bit Blocks

 

Carry-Lookahead Addition

- **Step 1:** Compute G_i and P_i for all columns
- **Step 2:** Compute G and P for k -bit blocks
- **Step 3:** C_{in} propagates through each k -bit propagate/generate logic (meanwhile computing sums)
- **Step 4:** Compute sum for most significant k -bit block

Carry-Lookahead Addition

- **Step 1:** Compute G_i and P_i for all columns

$$G_i = A_i B_i$$

$$P_i = A_i + B_i$$

Carry-Lookahead Addition


- **Step 1:** Compute G_i and P_i for all columns
- **Step 2:** Compute G and P for k -bit blocks

$$P_{3:0} = P_3 P_2 P_1 P_0$$

$$G_{3:0} = G_3 + P_3 (G_2 + P_2 (G_1 + P_1 G_0))$$


Carry-Lookahead Addition

 - **Step 1:** Compute G_i and P_i for all columns
- **Step 2:** Compute G and P for k -bit blocks
- **Step 3:** C_{in} propagates through each k -bit propagate/generate logic (meanwhile computing sums)




Carry-Lookahead Addition

 - **Step 1:** Compute G_i and P_i for all columns
- **Step 2:** Compute G and P for k -bit blocks
- **Step 3:** C_{in} propagates through each k -bit propagate/generate logic (meanwhile computing sums)
- **Step 4:** Compute sum for most significant k -bit block



32-bit CLA with 4-bit Blocks

 

Carry-Lookahead Adder Delay

For N -bit CLA with k -bit blocks:

$$t_{CLA} = t_{pg} + t_{pg_block} + (N/k - 1)t_{AND_OR} + kt_{FA}$$

- t_{pg} : delay to generate all P_i, G_i
- t_{pg_block} : delay to generate all $P_{i:j}, G_{i:j}$
- t_{AND_OR} : delay from C_{in} to C_{out} of final AND/OR gate in k -bit CLA block

An N -bit carry-lookahead adder is generally much faster than a ripple-carry adder for $N > 16$

Chapter 5: Digital Building Blocks

Prefix Addition

Prefix Adder

- Computes carry in (C_{i-1}) for each column, then computes sum:

$$S_i = (A_i \oplus B_i) \oplus C_{i-1}$$

- It computes C_{i-1} by:
 - Computing G and P for 1-, 2-, 4-, 8-bit blocks, etc. until all G_i (carry in) known
 - $G_i = C_i$
- $\log_2 N$ stages

Prefix Adder

- Carry out either *generated* in a column or *propagated* from a previous column.
- Column -1 holds C_{in} , so

$$G_{-1} = C_{in}, P_{-1} = X \text{ (not used)}$$

- Carry in to column i = carry out of column $i-1$:

$$C_{i-1} = G_{i-1:-1}$$

$G_{i-1:-1}$: generate signal spanning columns $i-1$ to -1

- Sum equation:

$$S_i = (A_i \oplus B_i) \oplus G_{i-1:-1}$$

- **Goal:** Quickly compute $G_{0:-1}, G_{1:-1}, G_{2:-1}, G_{3:-1}, G_{4:-1}, G_{5:-1}, \dots$
(called *prefixes*) $(= C_0, C_1, C_2, C_3, C_4, C_5, \dots)$

Prefix Adder

- Generate and propagate signals for a block spanning bits $i:j$

$$G_{i:j} = G_{i:k} + P_{i:k} G_{k-1:j}$$

$$P_{i:j} = P_{i:k} P_{k-1:j}$$

- In words:
 - **Generate:** block $i:j$ will generate a carry if:
 - **upper part** ($i:k$) generates a carry ($G_{i:k}$) **or**
 - upper part ($i:k$) propagates a carry ($P_{i:k}$) generated in lower part ($k-1:j$) ($G_{k-1:j}$)
 - **Propagate:** block $i:j$ will propagate a carry if *both* the upper and lower parts propagate the carry ($P_{i:k} \text{ AND } P_{k-1:j}$)

Prefix Adder Example

Step 1. Calculate P's and G's for **1-bit block**

$\overline{3\ 2\ 1\ 0\ -1}$	Column #
1 0 1 0	$A_{3:0}$
+ 0 1 1 1	$B_{3:0}$
1 1 1 1	$P_{3:3}, P_{2:2}, P_{1:1}, P_{0:0}$
0 0 1 0 1	$G_{3:3}, G_{2:2}, G_{1:1}, G_{0:0}, G_{-1:-1}$
$\uparrow$ C_{in} $\uparrow$ C_{in}	

Step 4. Continue to calculate P's and G's for larger blocks (8-bit, 16-bit, etc.)

Step 5. Use prefixes to calculate sums

$$C_{-1} = G_{-1:-1} = 1$$

$$C_0 = G_{0:-1} = 1$$

$$C_1 = G_{1:-1} = 1$$

$$C_2 = G_{2:-1} = 1$$

$$S_i = A_i \oplus A_i \oplus C_{i-1}$$

Step 2. Calculate P's and G's for **2-bit blocks**

$\overline{3\ 2\ 1\ 0\ -1}$	Column #
1 0 1 0	$A_{3:0}$
+ 0 1 1 1	$B_{3:0}$
	$P_{L:R} = P_L \bullet P_R$
	$G_{L:R} = G_L + P_L G_R$

0:-1 Block:

$$P_{0:-1} = X$$

$$G_{0:-1} = G_{0:0} + P_{0:0} G_{-1:-1}$$

$$= 0 + 1 \bullet 1$$

$$= 1$$

2:1 Block:

$$P_{2:1} = P_{2:2} P_{1:1} = 1 \bullet 1$$

$$G_{2:1} = G_{2:2} + P_{2:2} G_{1:1}$$

$$= 0 + 1 \bullet 1$$

$$= 1$$

Step 3. Calculate P's and G's for **4-bit blocks**

$\overline{3\ 2\ 1\ 0\ -1}$	Column #
1 0 1 0	$A_{3:0}$
+ 0 1 1 1	$B_{3:0}$
	$P_{L:R} = P_L \bullet P_R$
	$G_{L:R} = G_L + P_L G_R$

2:-1 Block:

$$P_{2:-1} = X$$

$$G_{2:-1} = G_{2:1} + P_{2:1} G_{0:-1}$$

$$= 1 + 1 \bullet 1$$

$$= 1$$

We calculate 3-bit spans too:

1:-1 Block:



$$P_{1:-1} = X$$

$$G_{1:-1} = G_{1:1} + P_{1:1} G_{0:-1}$$

$$= 1 + 1 \bullet 1$$

$$= 1$$

Prefix Adder Schematic

  

Prefix Adder Delay

$$t_{PA} = t_{pg} + \log_2 N (t_{pg_prefix}) + t_{XOR}$$

t_{pg} : delay to produce P_i, G_i (AND or OR gate)

t_{pg_prefix} : delay of black prefix cell (AND-OR gate)

Adder Delay Comparisons

Compare the delay of: 32-bit ripple-carry, CLA, and prefix adders

- CLA has 4-bit blocks
- 2-input gate delay = 100 ps; full adder delay = 300 ps

$$\begin{aligned}t_{\text{ripple}} &= Nt_{FA} = 32(300 \text{ ps}) \\ &= \mathbf{9.6 \text{ ns}}\end{aligned}$$

$$\begin{aligned}t_{CLA} &= t_{pg} + t_{pg_block} + (N/k - 1)t_{AND_OR} + kt_{FA} \\ &= [100 + 600 + (7)200 + 4(300)] \text{ ps} \\ &= \mathbf{3.3 \text{ ns}}\end{aligned}$$

$$\begin{aligned}t_{PA} &= t_{pg} + \log_2 N(t_{pg_prefix}) + t_{XOR} \\ &= [100 + \log_2 32(200) + 100] \text{ ps} \\ &= \mathbf{1.2 \text{ ns}}\end{aligned}$$


Chapter 5: Digital Building Blocks

Subtractors & Comparators


Subtractor

$$A - B = A + \overline{B} + 1$$

Symbol

 


Implementation

 


Comparator: Equality

Symbol

 


Implementation

 

Comparator: Signed Less Than

$A < B$ if $A - B$ is negative

Beware of overflow

 

Chapter 5: Digital Building Blocks

ALU:

Arithmetic Logic Unit

ALU: Arithmetic Logic Unit

ALU should perform:

- Addition
- Subtraction
- AND
- OR


ALU: Arithmetic Logic Unit

ALUControl _{1:0}	Function
00	Add
01	Subtract
10	AND
11	OR

Example: Perform $A \text{ OR } B$

$ALUControl_{1:0} = 11$

Result = $A \text{ OR } B$

 

ALU: Arithmetic Logic Unit

ALUControl _{1:0}	Function
00	Add
01	Subtract
10	AND
11	OR


Example: Perform $A \text{ OR } B$

$ALUControl_{1:0} = 11$

Mux selects output of OR gate as *Result*,

so:

$Result = A \text{ OR } B$

 

ALU: Arithmetic Logic Unit

ALUControl _{1:0}	Function
00	Add
01	Subtract
10	AND
11	OR

Example: Perform $A + B$

$ALUControl_{1:0} = 00$


$ALUControl_0 = 0$, so:

C_{in} to adder = 0

2nd input to adder is B


Mux selects *Sum* as *Result*, so

$Result = A + B$

 


ALU with Status Flags

Flag	Description
<i>N</i>	Result is N egative
<i>Z</i>	Result is Z ero
<i>C</i>	Adder produces C arry out
<i>V</i>	Adder o V erflowed

 

ALU with Status Flags

 


ALU with Status Flags: **N**egative


N = 1 if:

Result is **negative**

 So, *N* is connected to most significant bit of *Result*.




ALU with Status Flags: Zero

 

$Z = 1$ if:

all of the bits of *Result*
are 0

ALU with Status Flags: Carry

 

$C = 1$ if:

C_{out} of Adder is 1


AND

ALU is adding or subtracting (ALUControl is 00 or 01)


ALU with Status Flags: o**V**erflow

V = 1 if:

 The addition of 2 **same-signed numbers** produces a result with the **opposite sign**



ALU with Status Flags: o**V**erflow

 

V = 1 if:

ALU is performing addition or subtraction
($ALUControl_1 = 0$)

AND

A and Sum have opposite signs


AND

A and B have same signs for addition
($ALUControl_0 = 0$)

OR

A and B have different signs for subtraction
($ALUControl_0 = 1$)

ALU with Status Flags

 

Comparison based on Flags

Compare by subtracting and checking flags

Different for signed and unsigned


Comparison	Signed	Unsigned
==	Z	Z
!=	$\sim Z$	$\sim Z$
<	$N \wedge V$	$\sim C$
<=	$Z \mid (N \wedge V)$	$Z \mid \sim C$
>	$\sim Z \ \& \ \sim(N \wedge V)$	$\sim Z \ \& \ C$
>=	$\sim(N \wedge V)$	C

Other ALU Operations


- **Set Less Than** (also called Set if Less Than)
 - **Sets lsb** of result if $A < B$
 - Result = 0000...001 if $A < B$
 - Result = 0000...000 otherwise
 - Comes in signed and unsigned flavors
- **XOR**
 - Result = $A \text{ XOR } B$

Extending ALU: SLT

ALUControl _{2:0}	Function
00	add
01	subtract
10	and
11	or
	SLT

 

Fixing Overflow Error in SLT Logic

 

Chapter 5: Digital Building Blocks

Shifters, Multipliers, & Dividers

Shifters

Logical shifter: shifts value to left or right and fills empty spaces with 0's

- Ex: 11001 >> 2 = 00110
- Ex: 11001 << 2 = 00100

Arithmetic shifter: same as logical shifter, but on right shift, fills empty spaces with the old most significant bit (msb)


- Ex: 11001 >>> 2 = 11110
- Ex: 11001 <<< 2 = 00100

Rotator: rotates bits in a circle, such that bits shifted off one end are shifted into the other end


- Ex: 11001 ROR 2 = 01110
- Ex: 11001 ROL 2 = 00111

Shifter Design





Shift Left

 

Logical Shift Right

 

Arithmetic Shift Right

    

Shifters as Multipliers and Dividers

- $A \ll N = A \times 2^N$
 - Example: $00001 \ll 3 = 01000$ ($1 \times 2^3 = 8$)
 - Example: $11101 \ll 2 = 10100$ ($-3 \times 2^2 = -12$)
- $A \gg N = A \div 2^N$
 - Example: $01000 \gg 1 = 00100$ ($8 \div 2^1 = 4$)
 - Example: $10000 \gg 2 = 11100$ ($-16 \div 2^2 = -4$)

Multipliers

- **Partial products** formed by multiplying a single digit of the multiplier with multiplicand
- **Shifted** partial products **summed** to form result

Decimal

$$\begin{array}{r} 230 \\ \times 42 \\ \hline 460 \\ + 920 \\ \hline 9660 \end{array}$$

multiplicand
multiplier
partial
products
result


$$230 \times 42 = 9660$$

Binary

$$\begin{array}{r} 0101 \\ \times 0111 \\ \hline 0101 \\ 0101 \\ 0101 \\ + 0000 \\ \hline 0100011 \end{array}$$

$$5 \times 7 = 35$$

4 x 4 Multiplier

 

Dividers

$$A/B = Q + R/B$$

Decimal Example: $2584/15 = 172 \text{ R}4$

Long-Hand:

$$\begin{array}{r} 172 \text{ R}4 \\ 15 \overline{) 2584} \\ \underline{-15} \\ 108 \\ \underline{-105} \\ 34 \\ \underline{-30} \\ 4 \end{array}$$

Long-Hand Revisited:

$$\begin{array}{r} 0002 \\ -15 \\ \hline -13 \end{array} \quad \begin{array}{r} 0 \\ 3 \end{array} \begin{array}{r} 2 \\ 2 \end{array} \begin{array}{r} 1 \\ 1 \end{array} \begin{array}{r} 0 \\ 0 \end{array}$$
$$\begin{array}{r} 0025 \\ -15 \\ \hline 10 \end{array} \quad \begin{array}{r} 0 \\ 3 \end{array} \begin{array}{r} 1 \\ 2 \end{array} \begin{array}{r} 1 \\ 1 \end{array} \begin{array}{r} 0 \\ 0 \end{array}$$
$$\begin{array}{r} 0108 \\ -105 \\ \hline 3 \end{array} \quad \begin{array}{r} 0 \\ 3 \end{array} \begin{array}{r} 1 \\ 2 \end{array} \begin{array}{r} 7 \\ 1 \end{array} \begin{array}{r} 0 \\ 0 \end{array}$$
$$\begin{array}{r} 0034 \\ -30 \\ \hline 4 \end{array} \quad \begin{array}{r} 0 \\ 3 \end{array} \begin{array}{r} 1 \\ 2 \end{array} \begin{array}{r} 7 \\ 1 \end{array} \begin{array}{r} 2 \\ 0 \end{array}$$

Dividers

$$A/B = Q + R/B$$

Decimal: 2584/15 = 172 R4 **Binary:** 1101/0010 = 0110 R1

$$\begin{array}{r} 0002 \\ - 15 \\ \hline -13 \end{array}$$

$$\begin{array}{cccc} 0 & & & \\ \hline 3 & 2 & 1 & 0 \end{array}$$

$$\begin{array}{r} 0025 \\ - 15 \\ \hline 10 \end{array}$$

$$\begin{array}{cccc} 0 & 1 & & \\ \hline 3 & 2 & 1 & 0 \end{array}$$

$$\begin{array}{r} 0108 \\ - 105 \\ \hline 3 \end{array}$$

$$\begin{array}{cccc} 0 & 1 & 7 & \\ \hline 3 & 2 & 1 & 0 \end{array}$$

$$\begin{array}{r} 0034 \\ - 30 \\ \hline 4 \end{array}$$

$$\begin{array}{cccc} 0 & 1 & 7 & 2 \\ \hline 3 & 2 & 1 & 0 \end{array}$$

$$\begin{array}{r} 0001 \\ - 0010 \\ \hline 1111 \end{array}$$

$$\begin{array}{cccc} 0 & & & \\ \hline 3 & 2 & 1 & 0 \end{array}$$

$$\begin{array}{r} 0011 \\ - 0010 \\ \hline 0001 \end{array}$$

$$\begin{array}{cccc} 0 & 1 & & \\ \hline 3 & 2 & 1 & 0 \end{array}$$

$$\begin{array}{r} 0010 \\ - 0010 \\ \hline 0000 \end{array}$$

$$\begin{array}{cccc} 0 & 1 & 1 & \\ \hline 3 & 2 & 1 & 0 \end{array}$$

$$\begin{array}{r} 0001 \\ - 0010 \\ \hline 1111 \end{array}$$

$$\begin{array}{cccc} 0 & 1 & 1 & 0 \\ \hline 3 & 2 & 1 & 0 \end{array} \text{ R1}$$

Dividers

$$A/B = Q + R/B$$

$$R' = 0$$

for $i = N-1$ to 0

$$R = \{R' \ll 1, A_i\}$$

$$D = R - B$$

if $D < 0$, $Q_i = 0$; $R' = R$

else $Q_i = 1$; $R' = D$

$$R = R'$$

Binary: 1101/10 = 0110 R1


$$\begin{array}{r} 0001 \\ -0010 \\ \hline 1111 \end{array} \quad \begin{array}{r} 0 \\ \hline 3 \end{array} \begin{array}{r} \\ \hline 2 \end{array} \begin{array}{r} \\ \hline 1 \end{array} \begin{array}{r} \\ \hline 0 \end{array}$$

$$\begin{array}{r} 0011 \\ -0010 \\ \hline 0001 \end{array} \quad \begin{array}{r} 0 \\ \hline 3 \end{array} \begin{array}{r} 1 \\ \hline 2 \end{array} \begin{array}{r} \\ \hline 1 \end{array} \begin{array}{r} \\ \hline 0 \end{array}$$

$$\begin{array}{r} 0010 \\ -0010 \\ \hline 0000 \end{array} \quad \begin{array}{r} 0 \\ \hline 3 \end{array} \begin{array}{r} 1 \\ \hline 2 \end{array} \begin{array}{r} 1 \\ \hline 1 \end{array} \begin{array}{r} \\ \hline 0 \end{array}$$



$$\begin{array}{r} 0001 \\ -0010 \\ \hline 1111 \end{array} \quad \begin{array}{r} 0 \\ \hline 3 \end{array} \begin{array}{r} 1 \\ \hline 2 \end{array} \begin{array}{r} 1 \\ \hline 1 \end{array} \begin{array}{r} 0 \\ \hline 0 \end{array} \quad R1$$

4 x 4 Divider

 

Each row computes one iteration of the division algorithm.

Legend

  

Division: $A/B = Q + R/B$

$R' = 0$

for $i = N-1$ to 0

$R = \{R' \ll 1, A_i\}$


$D = R - B$

if $D < 0$, $Q_i = 0$, $R' = R$



else $Q_i = 1$, $R' = D$

$R = R'$

4 x 4 Divider

 

Legend

  

$$\begin{array}{r} 0001 \\ -0010 \\ \hline 1111 \end{array} \quad \begin{array}{r} 0 \\ 3 \quad 2 \quad 1 \quad 0 \end{array}$$

$$\begin{array}{r} 0011 \\ -0010 \\ \hline 0001 \end{array} \quad \begin{array}{r} 0 \quad 1 \\ 3 \quad 2 \quad 1 \quad 0 \end{array}$$

$$\begin{array}{r} 0010 \\ -0010 \\ \hline 0000 \end{array} \quad \begin{array}{r} 0 \quad 1 \quad 1 \\ 3 \quad 2 \quad 1 \quad 0 \end{array}$$

$$\begin{array}{r} 0001 \\ -0010 \\ \hline 1111 \end{array} \quad \begin{array}{r} 0 \quad 1 \quad 1 \quad 0 \\ 3 \quad 2 \quad 1 \quad 0 \end{array} \quad R1$$

Each row computes one iteration of the division algorithm.

Chapter 5: Digital Building Blocks

Fixed-Point Numbers

Number Systems

Numbers we can represent using binary representations

- **Positive numbers**
 - Unsigned binary
- **Negative numbers**
 - Two's complement
 - Sign/magnitude numbers

What about **fractions**?

Numbers with Fractions

Two common notations:

- **Fixed-point:** binary point fixed
- **Floating-point:** binary point floats to the right of the most significant 1

Fixed-Point Numbers

- 6.75 using 4 integer bits and 4 fraction bits:

01101100

0110.1100

$$2^2 + 2^1 + 2^{-1} + 2^{-2} = 6.75$$

- Binary point is implied
- The number of integer and fraction bits must be agreed upon beforehand

Unsigned Fixed Point Formats

- **Ua.b**: unsigned number with
 - **a** integer bits
 - **b** fractional bits.
- **Example: 6.75** is
 - **U4.4**: 01101100
 - **U3.5**: 11011000
 - **U6.2**: 00011011
- 8, 16, and 32-bit fixed point numbers are common
 - **U8.8** often represents sensor data, audio, pixels
 - **U16.16** used for higher precision signal processing

Signed Fixed Point Formats

- **Qa.b:** signed 2's complement number with
 - **a** integer bits (including the sign bit)
 - **b** fractional bits
- **To negate a Q fixed point number:**
 - Invert the bits
 - Add one to the LSB
- **Example:** write **-6.75** in Q4.4
 - 6.75 = 01101100
 - Invert: 10010011
 - Add 1 LSB: 10010100
- **Q1.15** (aka Q15) is common for signal processing (1, -1]

Saturating Arithmetic

- Fixed point **overflow** is usually bad
 - Produces undesired artifacts:
 - Video: dark pixel in middle of bright pixels
 - Audio: clicking sounds
- **Saturating arithmetic**
 - Instead of overflowing, use largest value
 - In U4.4: $11000000 + 01111000 = 11111111$
 $12 \quad \quad + 7.5 \quad \quad = 15.9375$

Chapter 5: Digital Building Blocks

Floating-Point Numbers

Floating-Point Numbers

- Binary point floats to the right of the most significant 1
- Similar to decimal scientific notation
- For example, write 273_{10} in scientific notation:

$$273 = 2.73 \times 10^2$$

- In general, a number is written in scientific notation as:


$$\pm \mathbf{M} \times \mathbf{B}^{\mathbf{E}}$$

- $\mathbf{M}$ = mantissa
- $\mathbf{B}$ = base
- $\mathbf{E}$ = exponent
- In the example, $M = 2.73$, $B = 10$, and $E = 2$

Floating vs. Fixed Point Numbers

- Floating point numbers are like **scientific notation**
 - Allow a **greater dynamic range** of smallest to largest
 - **Arithmetic is harder**
 - Mantissa must be aligned before adding
 - This costs performance and power
- Fixed point numbers are **harder for the programmer**
 - **Smaller dynamic range**
 - Take care of **overflow**
- **Floating Point** is preferred for general-purpose computing where programming time is most important
- **Fixed Point** is preferred for signal processing performance, power, and hardware cost matter most
 - Machine learning, video

Floating-Point Numbers

 

- **Example:** represent the value 228_{10} using a 32-bit floating point representation

We show three versions – **the final version** is called the:

IEEE 754 floating-point standard

Floating-Point Representation 1

1. Convert decimal to binary:


$$228_{10} = 11100100_2$$

2. Write the number in “binary scientific notation”:

$$11100100_2 = 1.11001_2 \times 2^7$$

 
3. Fill in each field of the 32-bit floating point number:

- The sign bit is positive (0)
- The 8 exponent bits represent the value 7
- The remaining 23 bits are the mantissa



Floating-Point Representation 2

 - First bit of the mantissa is always 1:
 - $228_{10} = 11100100_2 = \mathbf{1.11001} \times 2^7$
- So, no need to store it: *implicit leading 1*
- Store just **fraction bits** in 23-bit field



Floating-Point Representation 3


- **Biased exponent:** bias = 127 (01111111_2)

- Biased exponent = bias + exponent

- Exponent of 7 is stored as:

$$127 + 7 = 134 = 0x10000110_2$$

 - The **IEEE 754 32-bit floating-point representation** of 228_{10}



in hexadecimal: **0x43640000**

Floating-Point Example

Write -58.25_{10} in floating point (IEEE 754)

1. Convert magnitude of decimal to binary:

$$58.25_{10} = 111010.01_2$$

2. Write in binary scientific notation:


$$1.1101001 \times 2^5$$

3. Fill in fields:

Sign bit: 1 (negative)

8 exponent bits: $(127 + 5) = 132 = 10000100_2$

 23 fraction bits: 110 1001 0000 0000 0000 0000



in hexadecimal: **0xC2690000**

Floating-Point Special Cases

Number	Sign	Exponent	Fraction
0	X	00000000	0000000000000000000000000000
∞	0	11111111	0000000000000000000000000000
$-\infty$	1	11111111	0000000000000000000000000000
NaN	X	11111111	non-zero

Floating-Point Precision

- **Single-Precision:**

- 32-bit
- 1 sign bit, 8 exponent bits, 23 fraction bits
- bias = 127

- **Double-Precision:**

- 64-bit
- 1 sign bit, 11 exponent bits, 52 fraction bits
- bias = 1023

Floating-Point Rounding & Overflow

- **Overflow:** number too large to be represented
- **Underflow:** number too small to be represented
- **Rounding modes:**
 - Down
 - Up
 - Toward zero
 - To nearest
- **Example:** round 1.100101 (1.578125) to only 3 fraction bits
 - **Down:** 1.100
 - **Up:** 1.101
 - **Toward zero:** 1.100
 - **To nearest:** 1.101 (1.625 is closer to 1.578125 than 1.5 is)

Chapter 5: Digital Building Blocks

Floating-Point Addition

Floating-Point Addition

1. **Extract** exponent and fraction bits
2. **Prepend** leading 1 to form mantissa
3. **Compare** exponents
4. **Shift** smaller mantissa if necessary
5. **Add** mantissas
6. **Normalize** mantissa and adjust exponent if necessary
7. **Round** result
8. **Assemble** exponent and fraction back into floating-point format

Floating-Point Addition Example

Add the following floating-point numbers:

0x3FC00000

0x40500000

Floating-Point Addition Example

1. Extract exponent and fraction bits

	1 bit	8 bits	23 bits
0x3FC00000	0	01111111	100 0000 0000 0000 0000 0000
	Sign	Exponent	Fraction
	1 bit	8 bits	23 bits
0x40500000	0	10000000	101 0000 0000 0000 0000 0000
	Sign	Exponent	Fraction

For first number (N1): $S = 0, E = 127, F = .1$

For second number (N2): $S = 0, E = 128, F = .101$

2. Prepend leading 1 to form mantissa

N1: 1.1

N2: 1.101

Floating-Point Addition Example

3. Compare exponents

$127 - 128 = -1$, so shift N1 right by 1 bit

4. Shift smaller mantissa if necessary

shift N1's mantissa: $1.1 \gg 1 = 0.11$ ($\times 2^1$)

5. Add mantissas

$$\begin{array}{r} 0.11 \times 2^1 \\ + 1.101 \times 2^1 \\ \hline 10.011 \times 2^1 \end{array}$$

Floating-Point Addition Example

6. Normalize mantissa and adjust exponent if necessary

$$10.011 \times 2^1 = 1.0011 \times 2^2$$

7. Round result

No need (fits in 23 bits)

8. Assemble exponent and fraction back into floating-point format

$$S = 0, E = 2 + 127 = 129 = 10000001_2, F = 001100\dots$$

1 bit	8 bits	23 bits
0	10000001	001 1000 0000 0000 0000 0000
Sign	Exponent	Fraction

in hexadecimal: **0x40980000**


Chapter 5: Digital Building Blocks

Counters & Shift Registers


Counters

- Increments on each clock edge
- Used to cycle through numbers. For example,
 - 000, 001, 010, 011, 100, 101, 110, 111, 000, 001...
- **Example uses:**
 - Digital clock displays
 - Program counter: keeps track of current instruction executing

Symbol

 

Implementation

 

Counter SystemVerilog Idiom

```
module counter(input  logic      clk, reset,
               output logic [7:0] q);
```

```
    always_ff @(posedge clk)
        if (reset) q <= 0;    // synchronous reset
        else      q <= q+1; //
```

```
end
```

```
// alternative more verbose
```

```
module counter(input  logic      clk, reset,
               output logic [7:0] q);
```

```
    logic [7:0] nextq;
```

```
    assign nextq = q + 1; // adder
```

```
    always_ff @(posedge clk) // state register with synchronous reset
```

```
        if (reset) q <= 0;
```

```
        else      q <= nextq;
```

```
end
```

Divide-by- 2^N Counter

- Most significant bit of an N-bit counter toggles every 2^N cycles.
- Useful for slowing a clock. Ex: blink an LED
- Example: 50 MHz clock, 24-bit counter
 - 2.98 Hz


Digitally Controlled Oscillator

- N-bit counter
- Add p on each cycle, instead of 1
- Most significant bit toggles at $f_{\text{out}} = f_{\text{clk}} * p / 2^N$
- Example: $f_{\text{clk}} = 50 \text{ MHz}$ clock
 - How to generate a $f_{\text{out}} = 200 \text{ Hz}$ signal?
 - $p/2^N = 200 / 50 \text{ MHz}$
- Try $N = 24$, $p = 67 \rightarrow f_{\text{out}} = 199.676 \text{ Hz}$
- Or $N = 32$, $p = 17179 \rightarrow f_{\text{out}} = 199.990 \text{ Hz}$


Shift Registers

- Shift a new bit in on each clock edge
- Shift a bit out on each clock edge
- *Serial-to-parallel converter*: converts serial input (S_{in}) to parallel output ($Q_{0:N-1}$)

Symbol:

 


Implementation:

 

Shift Register with Parallel Load

 - When $Load = 1$, acts as a normal N -bit register
- When $Load = 0$, acts as a shift register
- Now can act as a *serial-to-parallel converter* (S_{in} to $Q_{0:N-1}$) or a *parallel-to-serial converter* ($D_{0:N-1}$ to S_{out})



Shift Register SystemVerilog Idiom

```
module shiftreg #(parameter N=8)
    (input  logic      clk,
     input  logic      reset, load,
     input  logic      sin,
     input  logic [N-1:0] d,
     output logic [N-1:0] q,
     output logic      sout);

    always_ff @(posedge clk, posedge reset)
        if (reset)      q <= 0;
        else if (load)   q <= d;
        else             q <= {q[N-2:0], sin};


    assign sout = q[N-1];
end
```

Chapter 5: Digital Building Blocks

Memory



Memory Arrays

 - Efficiently store large amounts of data
- M -bit data value read/written at each unique N -bit address
- 3 common types:
 - Dynamic random access memory (DRAM)
 - Static random access memory (SRAM)
 - Read only memory (ROM)



Memory Arrays

  
- 2-dimensional array of bit cells
- Each bit cell stores one bit
- N address bits and M data bits:
 - 2^N rows and M columns
 - **Depth:** number of rows (number of words)
 - **Width:** number of columns (size of word)
 - **Array size:** depth $\times$ width = $2^N \times M$




Address	Data			
11	0	1	0	depth ↑ ↓
10	1	0	0	
01	1	1	0	
00	0	1	1	
	width ←→			

Memory Array Example





 
- $2^2 \times 3$ -bit array
- Number of words: 4
- Word size: 3-bits
- For example, the 3-bit word stored at address 10 is 100



Memory Arrays

 

Memory Array Bit Cells

     


(a)

(b)

Memory Array

- **Wordline:**

 - like an enable
- single row in memory array read/written
- corresponds to unique address
- only one wordline **HIGH** at once



Types of Memory

- Random access memory (RAM): **volatile**
- Read only memory (ROM): **nonvolatile**

RAM: Random Access Memory

- **Volatile:** loses its data when power off
- Read and written quickly
- Main memory in your computer is RAM (DRAM)

Historically called *random access* memory because any data word accessed as easily as any other (in contrast to sequential access memories such as a tape recorder)

ROM: Read Only Memory

- **Nonvolatile:** retains data when power off
- Read quickly, but writing is impossible or slow
- Flash memory in cameras, thumb drives, and digital cameras are all ROMs

Historically called *read only* memory because ROMs were written at time of fabrication or by burning fuses. Once a ROM was configured, it could not be written again. This is no longer the case for Flash memory and other types of ROMs.

Chapter 5: Digital Building Blocks

RAM

Types of RAM

- **DRAM** (Dynamic random access memory)
- **SRAM** (Static random access memory)
- Differ in how they store data:
 - DRAM uses a capacitor
 - SRAM uses cross-coupled inverters



Robert Dennard, 1932 -

- Invented DRAM in 1966 at IBM
- Others were skeptical that the idea would work
- By the mid-1970's DRAM in virtually all computers





DRAM

 
 
- Data bits stored on **capacitor**
- *Dynamic* because the value needs to be **refreshed** (rewritten) periodically and after read:
 - Charge leakage from the capacitor degrades the value
 - Reading destroys the stored value




DRAM

  


SRAM

  


Memory Arrays Review

 

DRAM bit cell:

 



SRAM bit cell:

 


Chapter 5: Digital Building Blocks

ROM

ROM: Dot Notation

  

ROM Storage

 


Address	Data			depth ↑ ↓
11	0	1	0	
10	1	0	0	
01	1	1	0	
00	0	1	1	
width ←→				

Fujio Masuoka, 1944 -

- Developed memories and high speed circuits at Toshiba, 1971-1994
- Invented Flash memory as an unauthorized project pursued during nights and weekends in the late 1970's
- The process of erasing the memory reminded him of the flash of a camera
- Toshiba slow to commercialize the idea; Intel was first to market in 1988
- Flash has grown into a \$25 billion per year market



ROM Logic

 

$$Data_2 = A_1 \oplus A_0$$


$$Data_1 = \bar{A}_1 + A_0$$

$$Data_0 = \bar{A}_1 \bar{A}_0$$

 Example: Logic with ROMs

Implement the following logic functions using a $2^2 \times 3$ -bit ROM:


- $X = AB$
- $Y = A + B$
- $Z = A \overline{B}$



 
Example: Logic with ROMs

Implement the following logic functions using a $2^2 \times 3$ -bit ROM:

- $X = AB$
- $Y = A + B$
- $Z = A \overline{B}$



Logic with Any Memory Array

 


$Data_2 =$

$Data_1 =$

$Data_0 =$

Logic with Any Memory Array

 

$$Data_2 = A_1 \oplus A_0$$


$$Data_1 = \bar{A}_1 + A_0$$

$$Data_0 = \bar{A}_1 \bar{A}_0$$

Logic with Memory Arrays

Implement the following logic functions using a $2^2 \times 3$ -bit memory array:

 
- $X = AB$
- $Y = A + B$
- $Z = A \overline{B}$



Logic with Memory Arrays

Implement the following logic functions using a $2^2 \times 3$ -bit memory array:

 
- $X = AB$
- $Y = A + B$
- $Z = A \overline{B}$



Logic with Memory Arrays

Called *lookup tables* (**LUTs**): look up output at each input combination (address)

Truth Table		
A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

 

Chapter 5: Digital Building Blocks

SystemVerilog & Multiported Memories

SystemVerilog RAM

```
// 256 x 3 RAM with one read/write port
module ram(input logic      clk, we,
           input logic [7:0] a,
           input logic [2:0] wd,
           output logic [2:0] rd);

    logic [2:0] RAM[255:0];

    assign rd = RAM[a];

    always @(posedge clk)
        if (we)
            RAM[a] <= wd;
endmodule
```

SystemVerilog ROM

```
// 128 x 32 ROM with one read port
// Contents initialized from file
module rom(input  logic [6:0]  a,
           output logic [31:0] rd);

    logic [31:0] ROM[127:0];

    // initialize contents from file
    initial
        $readmemh("memfile.dat", ROM);


    // read port
    assign rd = ROM[a];
endmodule
```

SystemVerilog ROM memfile

```
// memfile.dat
// Contains up to 128 lines of 32-bit hex numbers
// defining the contents of the ROM
01234567
89ABCDEF
FFFFFFFF
A5A5A5A5
...
```

Multi-ported Memories

 - **Port:** address/data pair
- 3-ported memory
 - 2 read ports (A1/RD1, A2/RD2)
 - 1 write port (A3/WD3, WE3 enables writing)
- **Register file:** small multi-ported memory



SystemVerilog Memory Arrays

```
// 32 x 32 register file with 2 read, 1 write port
// register 0 hardwired to read as 0
module regfile(input  logic          clk,
               input  logic          we3,
               input  logic [4:0]    ra1, ra2, wa3,
               input  logic [31:0]   wd3,
               output logic [31:0]   rd1, rd2);

    logic [31:0] rf[31:0];

    always_ff @(posedge clk)
        if (we3) rf[wa3] <= wd3;

    assign rd1 = (ra1 == 5'b00000) ? 32'b0 : rf[ra1];
    assign rd2 = (ra2 == 5'b00000) ? 32'b0 : rf[ra2];
endmodule
```

Chapter 5: Digital Building Blocks


Logic Arrays: PLAs & FPGAs

Logic Arrays

- **PLAs** (Programmable logic arrays)
 - AND array followed by OR array
 - Combinational logic only
 - Fixed internal connections
- **FPGAs** (Field programmable gate arrays)
 - Array of Logic Elements (LEs)
 - Combinational and sequential logic
 - Programmable internal connections


PLAs: Programmable Logic Arrays

 - $X = \overline{A}\overline{B}C + A\overline{B}C$
- $Y = A\overline{B}$



PLAs: Dot Notation


- $X = ABC + \bar{A}BC$
- $Y = AB$

 

FPGAs: Field Programmable Gate Arrays

- Composed of:
 - **LEs** (Logic elements): perform logic
 - **IOEs** (Input/output elements): interface with outside world
 - **Programmable interconnection:** connect LEs and IOEs
 - Some FPGAs include other building blocks such as multipliers and RAMs


General FPGA Layout

 

LE: Logic Element

- Composed of:
 - **LUTs** (lookup tables): perform combinational logic
 - **Flip-flops**: perform sequential logic
 - **Multiplexers**: connect LUTs and flip-flops

Altera Cyclone IV LE

 

From Cyclone IV datasheet

Altera Cyclone IV LE

- **The Altera Cyclone IV LE has:**
 - 1 four-input **LUT**
 - 1 **registered output**
 - 1 **combinational output**

LE Configuration Example

Show how to configure a Cyclone IV LE to perform the following functions:

- $X = \overline{A}\overline{B}C + A\overline{B}C$
- $Y = A\overline{B}$


LE Configuration Example

Show how to configure a Cyclone IV LE to perform the following functions:


$$- X = \overline{A}\overline{B}C + A\overline{B}\overline{C}$$

$$- Y = A\overline{B}$$

(A) data 1	(B) data 2	(C) data 3	data 4	(X) LUT output
0	0	0	X	0
0	0	1	X	1
0	1	0	X	0
0	1	1	X	0
1	0	0	X	0
1	0	1	X	0
1	1	0	X	1
1	1	1	X	0

 

(A) data 1	(B) data 2	data 3	data 4	(Y) LUT output
0	0	X	X	0
0	1	X	X	0
1	0	X	X	1
1	1	X	X	0

 

Logic Elements Example 1

How many Cyclone IV LEs are required to build

$$Y = A1 \oplus A2 \oplus A3 \oplus A4 \oplus A5 \oplus A6$$

Solution:

Logic Elements Example 1

How many Cyclone IV LEs are required to build

$$Y = A1 \oplus A2 \oplus A3 \oplus A4 \oplus A5 \oplus A6$$

Solution:

2 LEs

First computes $Y1 = A1 \oplus A2 \oplus A3 \oplus A4$ (function of 4 variables)

Second computes $Y = Y1 \oplus A5 \oplus A6$ (function of 3 variables)

Logic Elements Example 2

How many Cyclone IV LEs are required to build

32-bit 2:1 multiplexer

Solution:

Logic Elements Example 2

How many Cyclone IV LEs are required to build

32-bit 2:1 multiplexer

Solution:

32 LEs

A 1-bit mux is a function of 3 variables and fits in one LE

A 32-bit mux requires 32 copies

Logic Elements Example 3

How many Cyclone IV LEs are required to build

Arbitrary FSM with 2 bits of state, 2 inputs, 3 outputs

Solution:

Logic Elements Example 2

How many Cyclone IV LEs are required to build

32-bit 2:1 multiplexer

Solution:

32 LEs

A 1-bit mux is a function of 3 variables and fits in one LE

A 32-bit mux requires 32 copies

FPGA Design Flow

Using a CAD tool (such as Altera's Quartus II)

- **Enter the design** using schematic entry or an HDL
- **Simulate** the design
- **Synthesize** design and map it onto FPGA
- **Download the configuration** onto the FPGA
- **Test** the design

About these Notes

Digital Design and Computer Architecture Lecture Notes

© 2021 Sarah Harris and David Harris

These notes may be used and modified for educational and/or non-commercial purposes so long as the source is attributed.