

CA Quiz

Fahad Bin Faizal

23-06-16

Section G

Q1 A = 10100 B = 11 R' = 0 N = 5

N = 4

R' = 01

R = 01

D = ~~110~~ 110 < 0

Q_i = 0

R' = 01

N = 3

R' = 010

R = 010

D = 1011 < 0

Q_i = 0

R' = 010

N = 2

R' = 101

R = 101

D = 0010 ≥ 0

Q_i = 1

R' = 0010

N = 1

R' = 100

R = 100

D = 0001 ≥ 0

Q_i = 1

R' = 0001

N = 0

R' = 10

R = 10

D = 1110 < 0

Q_i = 0

R' = 0010

Q = 00110

R = 00010

Q2 $G_i = A_i \cdot B_i$
 $P_i = A_i \oplus B_i$

$C_i = G_i + P_i \cdot C_{i-1}$

Q3 Circuit : ALU

Control	Function
00	Add
01	Subtract
10	AND
11	OR

