

Computer Architecture- Quiz #6 -E


Name: _____ Roll#: _____ Section: _____

Total Time: 10 minutes

Total Marks: 12

8th April, 2026

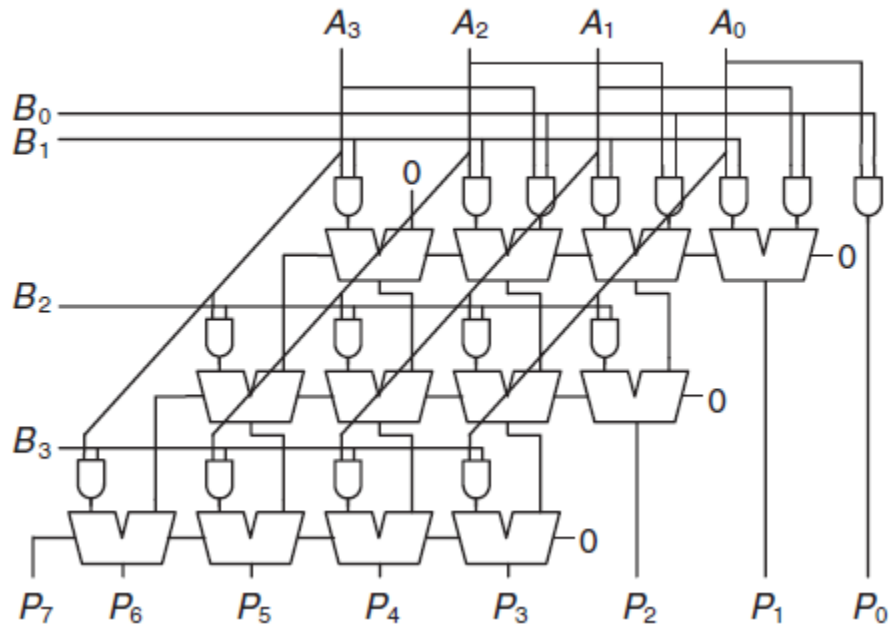Name the following diagram as discussed in the class.



Now write the equations for P_0 , P_3 and P_6