

Computer Architecture- Quiz #5-C

Name: _____ Roll#: _____

Section: _____

Total Time: 20 minutes

Total Marks: 20

7th April, 2026

CLO 2:

Question 1

Marks 15

Propagation delay of a TTL based Full adder is approximately **10 ns**. Calculate delay for a **16-bit ripple carry adder** based on TTL based full adders? **(2)**

Consider **Carry-Lookahead Adder** and Write generic single Bit expressions for generate (G_i), propagate (P_i) signals and Carryout signals. **(3)**

$G_i =$ _____, $P_i =$ _____

$C_i =$ _____

Calculate Column propagate P_i and generate signals G_i for each column if A = 11001, B = 10111

For a **4-bit carry look-ahead adder**, derive the expressions for the block propagate $P_{3:0}$ and block generate $G_{3:0}$ signals. Also, express the carry-out C_3 in terms of these block propagate and generate signals. **(5)**

$P_{3:0} =$ _____

$G_{3:0} =$ _____

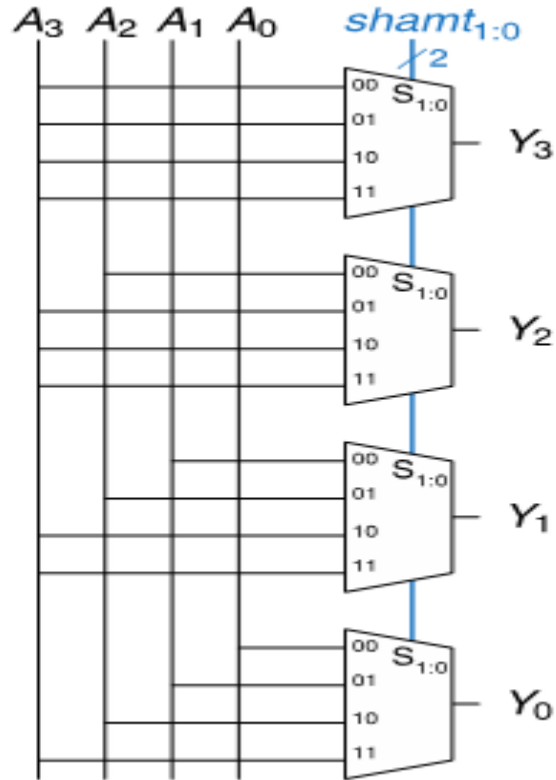
$C_3 =$ _____

CLO 2:

Question 2

Marks 5

Consider the given circuit. Evaluate its operation for input $A = 10$ and shift amount $shamt = 2$. Determine the final output $Y_{0:3}$ value in decimal form and identify the type of the circuit.

 $Y_{0:3} =$

Name:

CLO 2:

Question 3

Marks 5

Design a 2 x 2 multiplier?

