

Computer Architecture- Quiz #5-G

Name: _____ Roll#: _____

Section: _____

Total Time: 20 minutes

Total Marks: 20

7th April, 2026

CLO 2:

Question 1

Marks 10

Consider the algorithm given below run it for value where A =10100, B = 11

$$A/B = Q + R/B$$

$$R' = 0$$

for $i = N-1$ to 0

$$R = \{R' \ll 1, A_i\}$$

$$D = R - B$$

if $D < 0$, $Q_i = 0$; $R' = R$

else $Q_i = 1$; $R' = D$

$$R = R'$$

Initialization	A = _____, B = _____, $Q_i =$ _____ $R' =$ _____, N = _____, R = _____, D = _____
N = 4	A = _____, B = _____, $Q_i =$ _____ $R' =$ _____, N = _____, R = _____, D = _____
N = 3	A = _____, B = _____, $Q_i =$ _____ $R' =$ _____, N = _____, R = _____, D = _____
N = 2	A = _____, B = _____, $Q_i =$ _____ $R' =$ _____, N = _____, R = _____, D = _____
N = 1	A = _____, B = _____, $Q_i =$ _____ $R' =$ _____, N = _____, R = _____, D = _____
N = 0	A = _____, B = _____, $Q_i =$ _____ $R' =$ _____, N = _____, R = _____, D = _____

Final $Q_{4:0} =$ _____, R = _____

CLO 2:

Question 2

Marks 5

Consider **Carry-Lookahead Adder** and Write generic single Bit expressions for generate (G_i), propagate (P_i) signals and Carryout signals.

$G_i =$, $P_i =$


$C_i =$

CLO 2:

Question 3

Marks 5

Identify the **type of circuit** given below. Name all the unidentified inputs and outputs. Identify **CONTROL** bits and based on control bits fill the given **table**

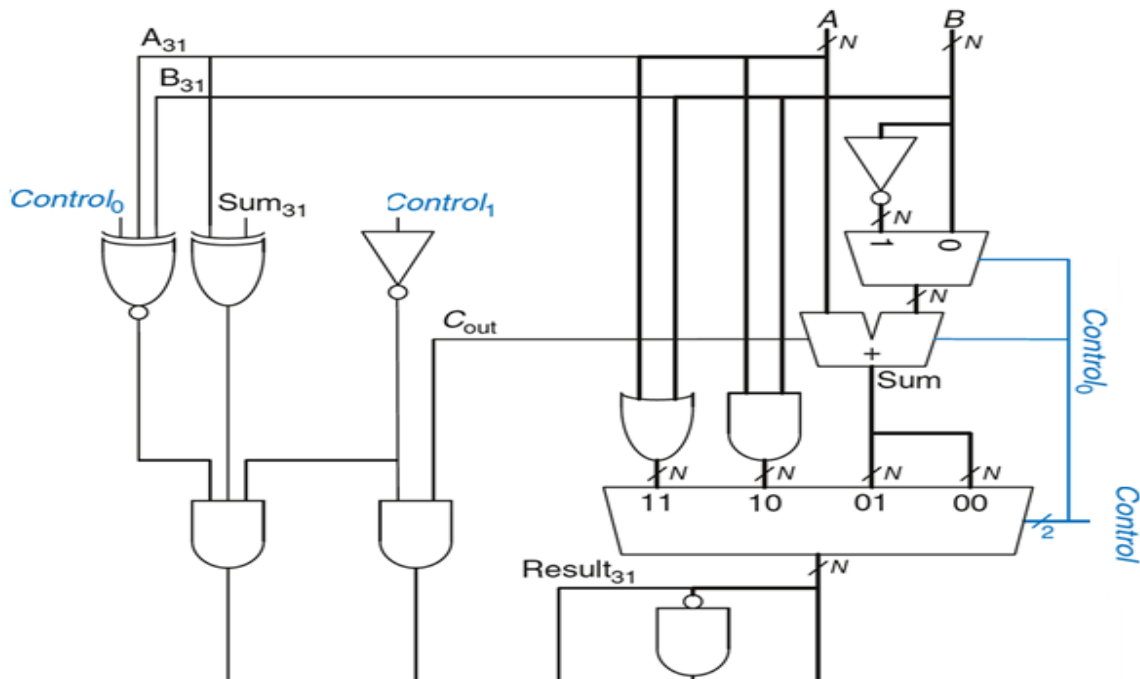

CONTROL 1:0	FUNCTION

Circuit Name: